

COA LAB(INTERNAL)

NAME- SHIVANSHU PATEL


ROLL NO -2300290120236

- a) Implementation of 4×1 Multiplexer and 2×4 Decoder on simulator as well as Hardware Chip
- b) Implementation of 8×1 Multiplexer and 3×8 Decoder on simulator as well as Hardware Chip.

DECODER (2×4)


A decoder is a device that converts an input, such as a digital signal, into an output that humans can understand.

2×4

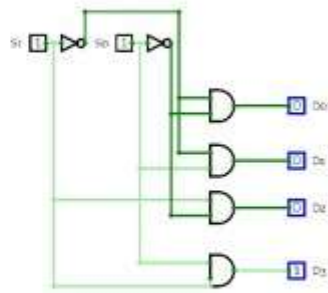

MULTIPLEXER(4*1)

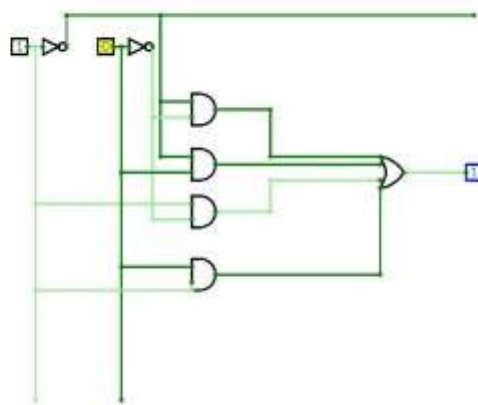A multiplexer (MUX) is a device that selects an input signal from multiple inputs and forwards it to a single output line. It is also known as a data selector. 4X1



4-to-1 Multiplexer

A **Multiplexer (MUX)** is a combinational circuit that selects one of several input signals and forwards the selected input to a single output line. A **4-to-1 MUX** has 4 input lines, 2 control lines (select lines), and 1 output line.

- **Inputs:**

- 4 data inputs: I_0, I_1, I_2, I_3
- 2 select lines: S_0, S_1

- **Output:**

- 1 output: Y